

# Knowledge Organiser

Years 6

Subject: Science Learning: Electricity

Key knowledge	
Understand how electricity works and how its power can vary	Date of Learning
Know that the brightness of a bulb is associated with the voltage	
Compare and give reasons for variations in how components function	
Use recognised symbols when representing a simple circuit in a diagram	
Construct simple series circuits	
Be able to answer questions about what happens when they try different components, for example; switches, bulbs, buzzers and motors	

Vocabulary	
<b>series circuits</b>	Is a circuit that has more than one resistor, but only one path through which the electricity (electrons) flows
<b>cells</b>	Is a device that is used to generate electricity, or one that is used to make chemical reactions possible by applying electricity
<b>generator</b>	A machine that converts energy into electricity
<b>turbine</b>	A machine that creates continuous power in which a wheel, or something similar, moves round and round by fast moving water, steam, gas or air
<b>fuses</b>	These are safety devices. They are strips of wire that melt and break an electric circuit if it goes over a safe level
<b>socket</b>	A safe device to plug your electrical items into at home. Almost every room at home will have at least one socket

Component	Symbol	Purpose
Cell (Battery)		Provides electrical energy
Power supply		Alternative to using cells
Wire		Allows current to travel
Bulb/light		Converts electrical energy into heat and light
Motor		Converts electrical energy into movement energy
Buzzer		Converts electrical energy into sound energy
Switch		Allows circuit to be opened or closed



**Prior Knowledge –**

**How electricity works, its importance in the home and knowledge of constructing a simple circuit.  
Renewable energy and its use over use of fossil fuels.  
Identify the difference and give examples of conductors and insulators.**